

What will be the output of an OR-gate if it has inputs 0 and 1?

VuAnswers.com

Answer (Please select your correct option)

- ☐ 0
- ☒ 1
- ☐ 2
- ☐ 3

correct

Made by: Waqar Siddhu