

What is the output state of an AND gate if the inputs are 0 and 1?

VuAnswers.com

Answer (Please select your correct option)

☐ 0

correct

☐ 1

☐ 2

☐ 3

Made by: Waqar Siddhu