

How many input signals are required for an OR-gate?

VuAnswers.com

Answer (Please select your correct option)

☐ 2

correct

☐ 8

☐ All multiples of two

☐ 1

Made by: Waqar Siddhu