

How many input signals are required for an OR-gate?

VuAnswers.com

Answer (Please select your correct option)

- ☒ 2 correct
- ☐ 8
- ☐ All multiples of two
- ☐ 1

Made by: Waqar Siddhu