

A circuit with two input signals and one output signal is called

VuAnswers.com

Answer (Please select your correct option)



NOT-gate (or inverter)



AND- gate

correct



None of these

Made by: Waqar Siddhu